



**Course Name:** EMBEDDED SYSTEMS I / III

**Course Number and Section:** 14:332:493:03 / 16:332:579:05

**Year:** Spring 2024

**Lab Report #:** 2

**Lab Instructor:** Milton Diaz

**Student Name and RUID:** Ruben Alias 207005068


**Date Submitted:** 03/01/2024

**GitHub Link:**

<https://github.com/embedded-systems-1-spring-2024-labs/lab-2-Herxity>


**Purpose/Objective:** The purpose of this lab was to design an Arithmetic Logic unit capable of 4-bit calculations, 16 total. It required opcode decoding, as well as loading calculations into registers.

**Theory of Operation:**

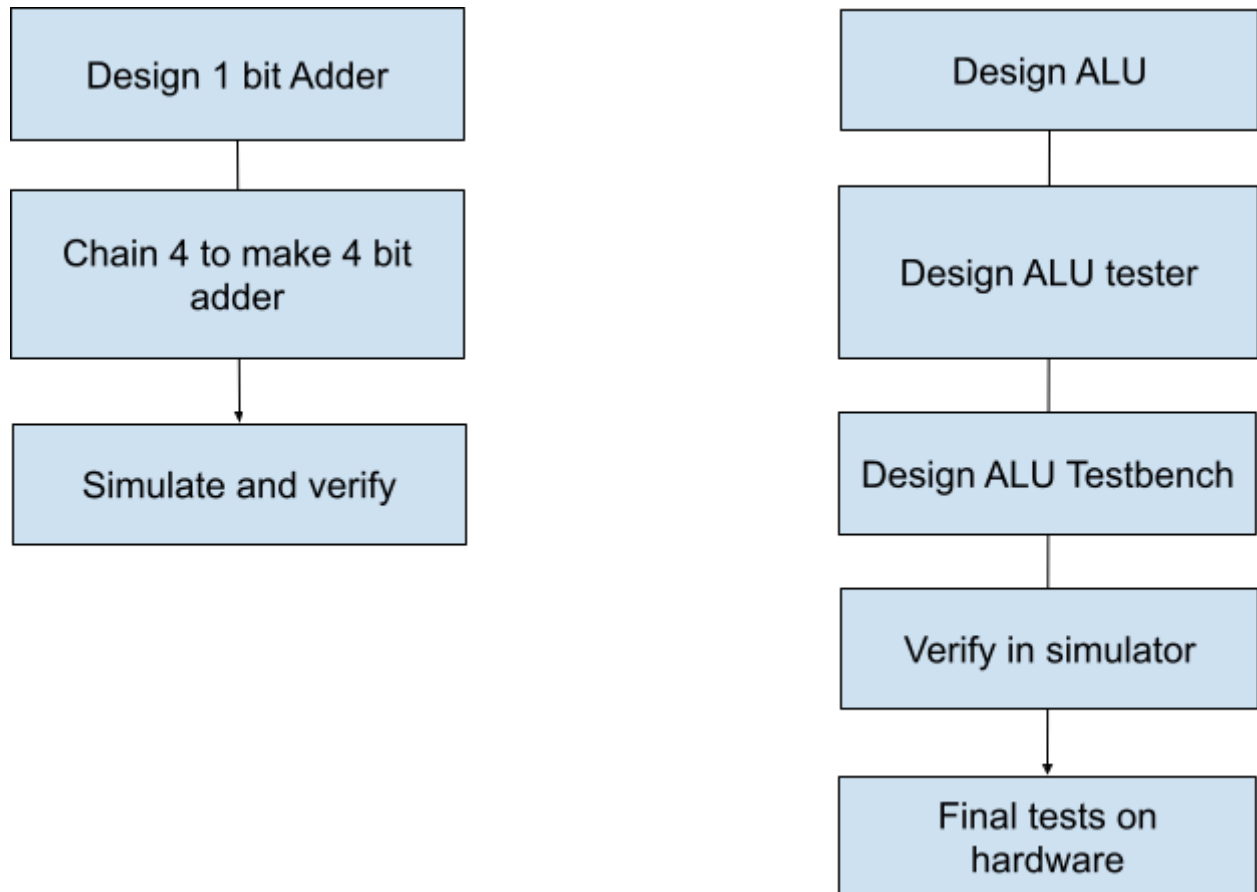


## Simulation Waveforms:

### Ripple Adder Sim

 

Testbench(This is just a test of basic ability to perform the calculations, in the absence of debouncing due to time):

#### 1. Subtraction

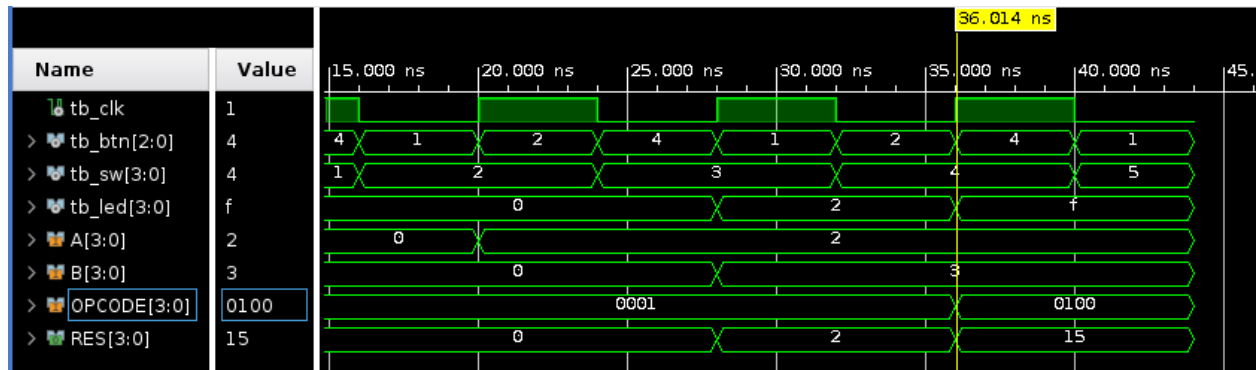

A = 2


B = 3

OPCODE = 0001

RES = 15

0010 - 0011 = 1111

#### 2. 0-A

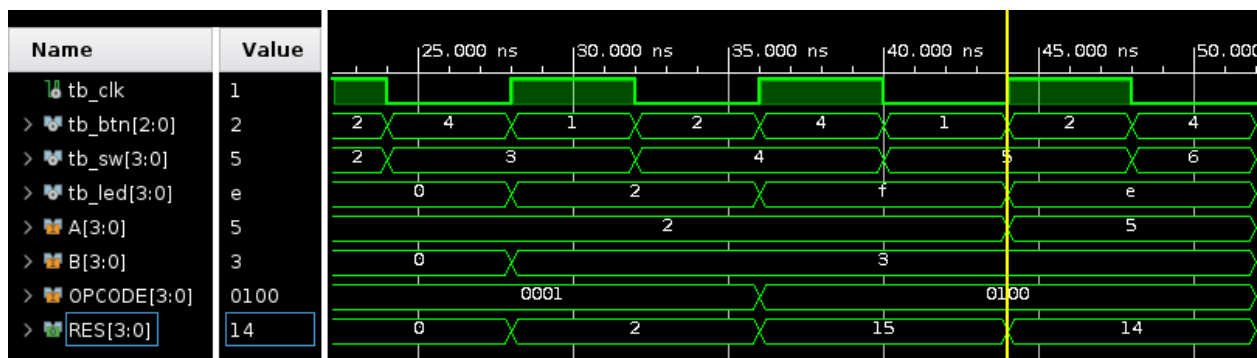


A = 2

B = 3

OPCODE = 0100

0-2=14

### 3. Shift Right

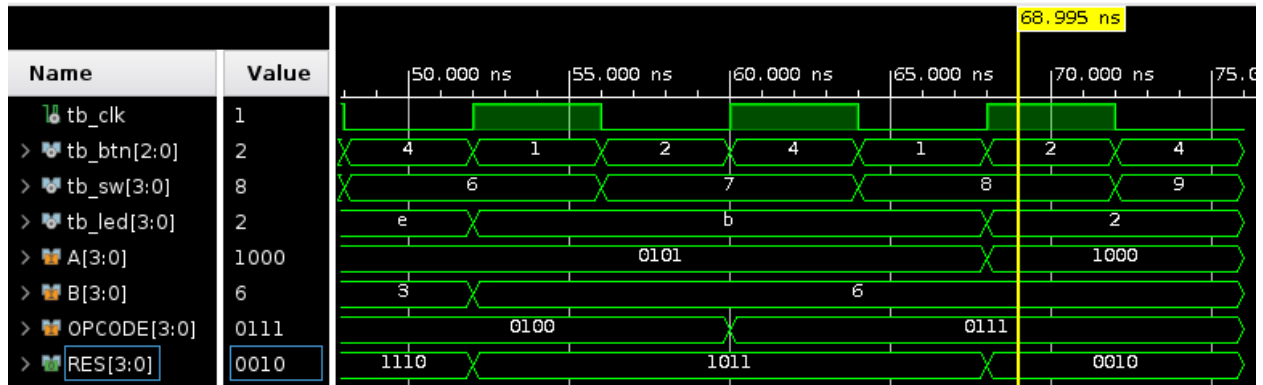

A = 0101


B = 1110

OPCODE = 0111

RES = 0010

Shifting right the bits of 0101 by 1, and padding a 0, yields 0010

### 4. Bitwise AND

 

A = 1000


B = 1001

**OPCODE = 1010**

**RES = 1000**

Bitwise and of 1000 and 1001 would yield 1000 as the 1's of both bits match then

## 5. Bitwise XNOR

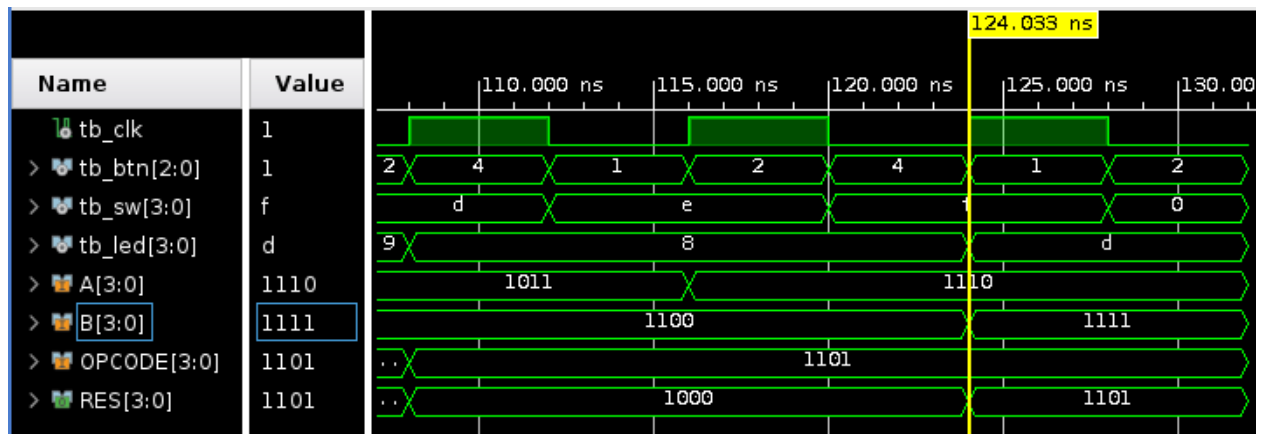

**A = 1110**


**B = 1100**

**OPCODE = 1101**

**RES = 1101**


Bitwise XNOR of 1110 and 1100 is 1101 as 1 xnor 1 =1 and 0 xnor 0 is 1, all other cases being 0.

## 6. A -1

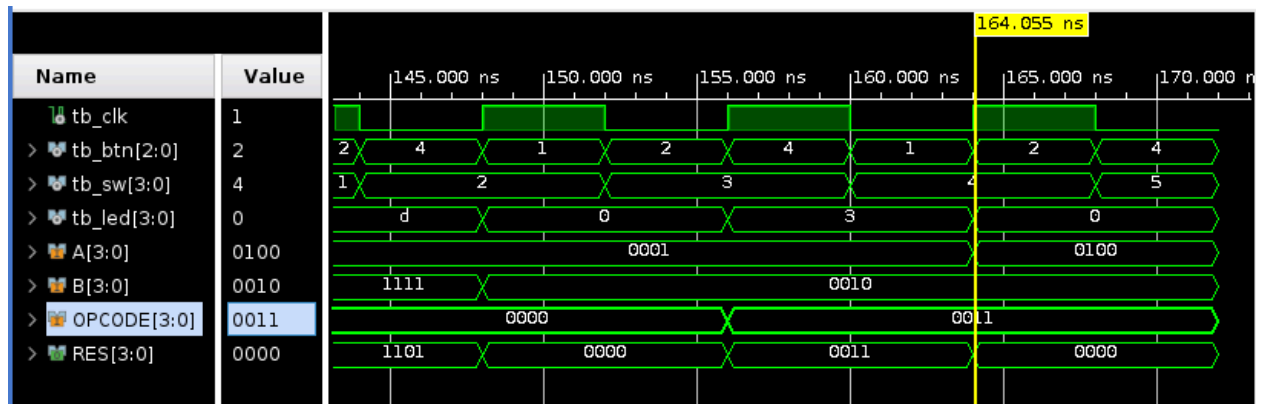

**A = 0001**  
**B = 0010**  
**OPCODE = 0011**  
**RES = 0000**  
**0001 - 1 = 0000**


## 7. Shift Left

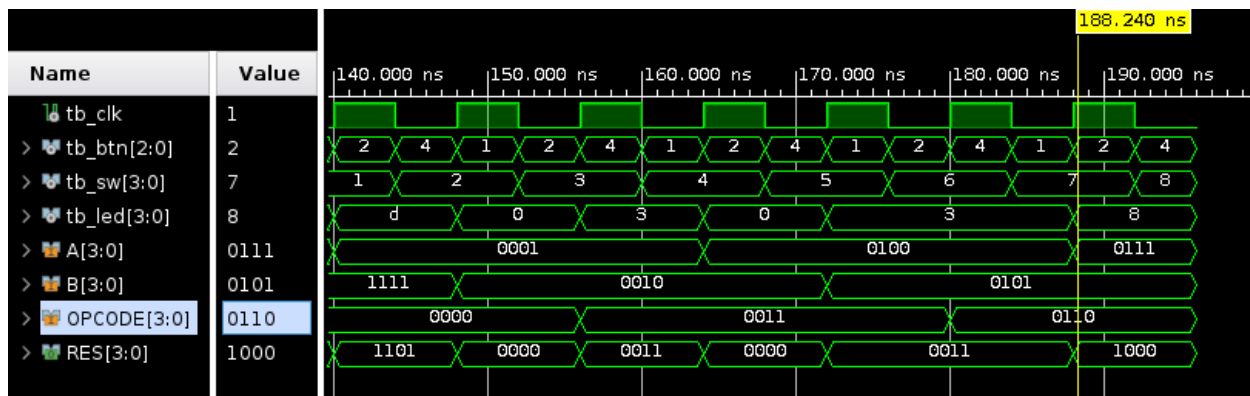

**A = 0100**  
**B = 0101**  
**OPCODE = 0110**  
**RES = 1000**

Shifting 0100 to the left by 1 bit and padding a 0 yields 1000

## 8. Not A

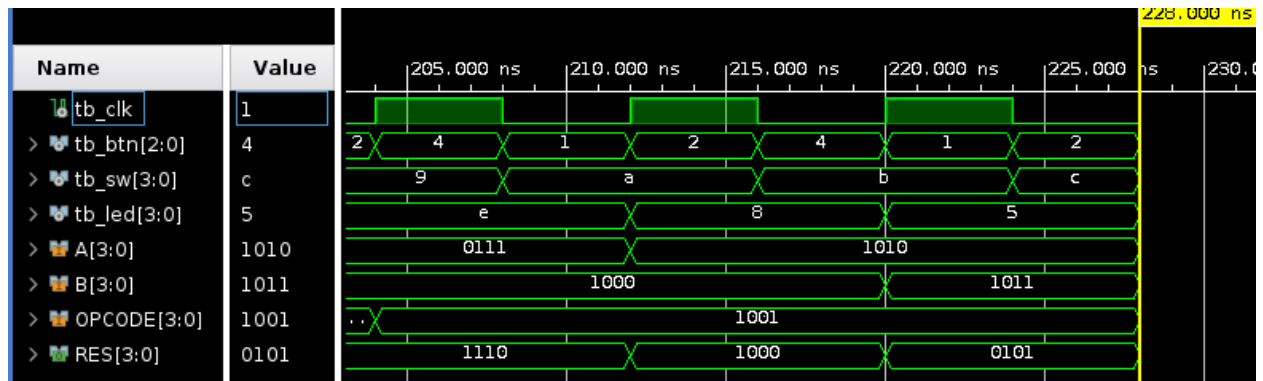


**A = 1010**  
**B = 1000**

**OPCODE = 1001**

**RES = 0101**

Inverting all the bits of A will convert each 0 to a 1 and vice versa.

### 9. A xnor B

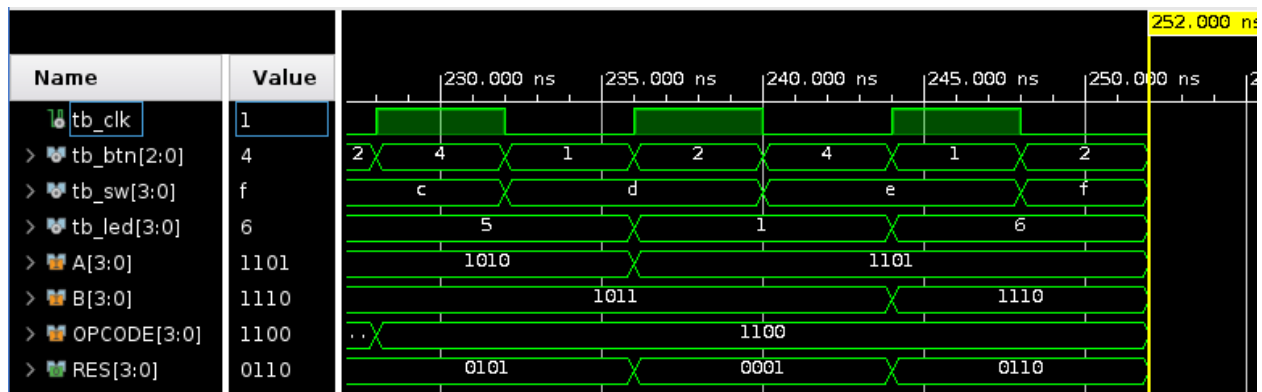

**A = 1101**


**B = 1011**

**OPCODE = 1100**

**RES = 0110**

The 1's on the ends will turn to 0s in the output, whereas the alternating 10 and 01 in the middle of each input will be converted to 1's, hence 0110

### 10. A nor B

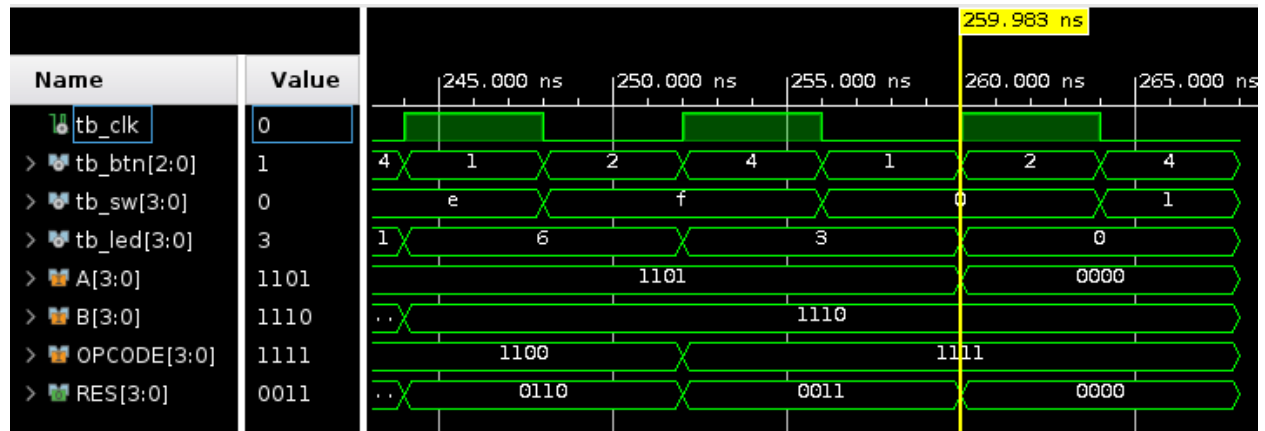

A = 1101


B = 1110

OPCODE = 1111

RES = 0000

Because there are no indices where both bits are 0 in A or B, all the output bits are 0.

## 11. A > B

 

A = 0011

B = 0100


OPCODE = 0101

RES = 0000

Since A is not greater than B, the output is 0000 rather than 0001

## 12. Shift right arithmetic



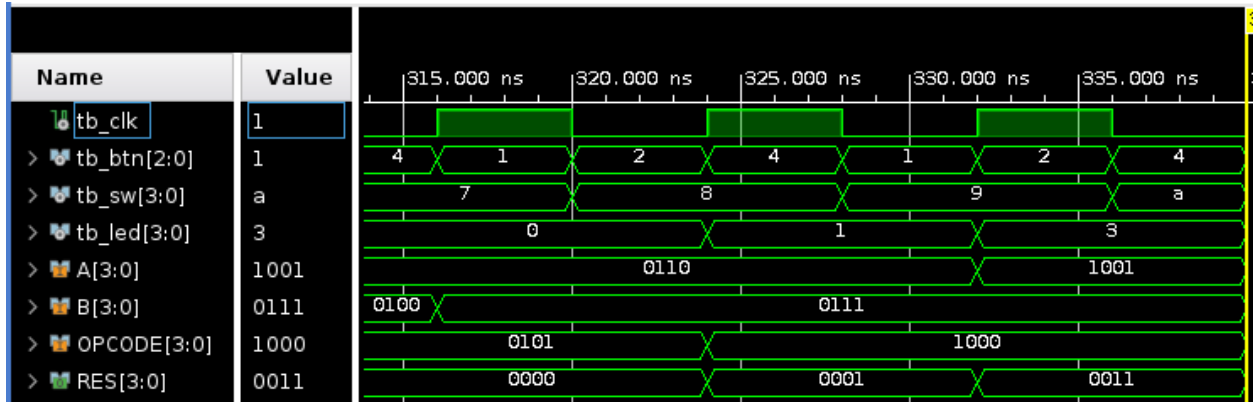

A = 0110


B = 0111

OPCODE = 1000

RES = 0011

The output is 0011, which is both shifted right and the sign of the number is preserved as well.

### 13. A OR B

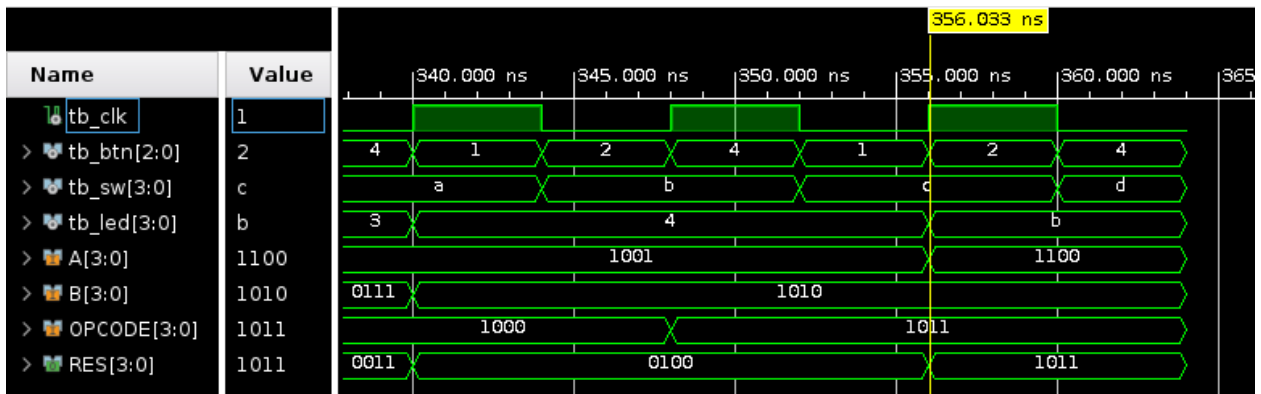

A = 1001

B = 1010

OPCODE = 1011


RES = 1011

1001 OR 1010 = 1011


## Vivado Schematics:

### One-Bit Full Adder


#### RTL Schematic

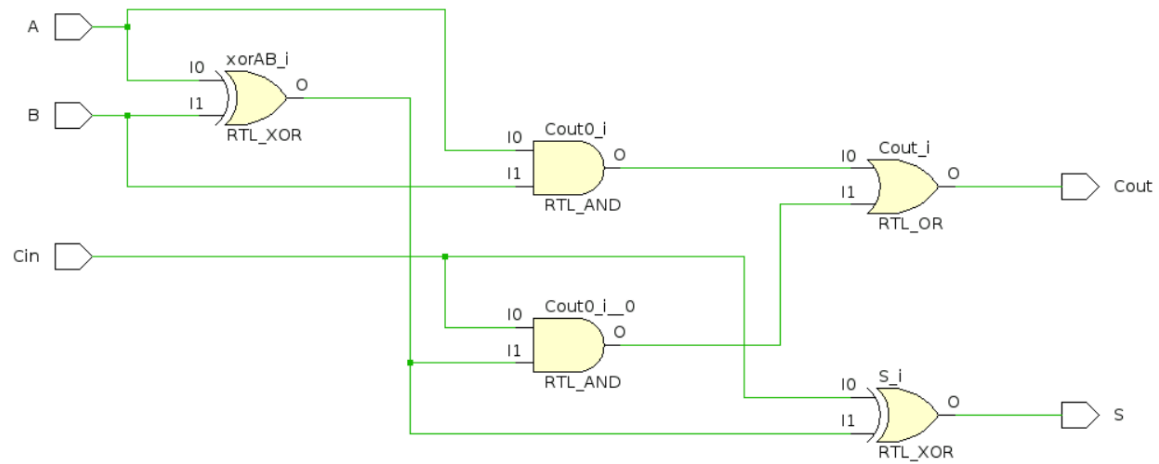

#### Synthesis Schematic

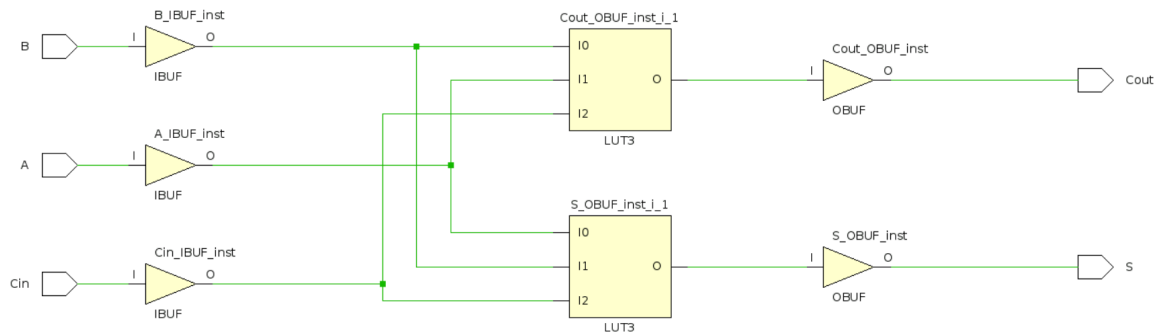

#### On-Chip Power Graph

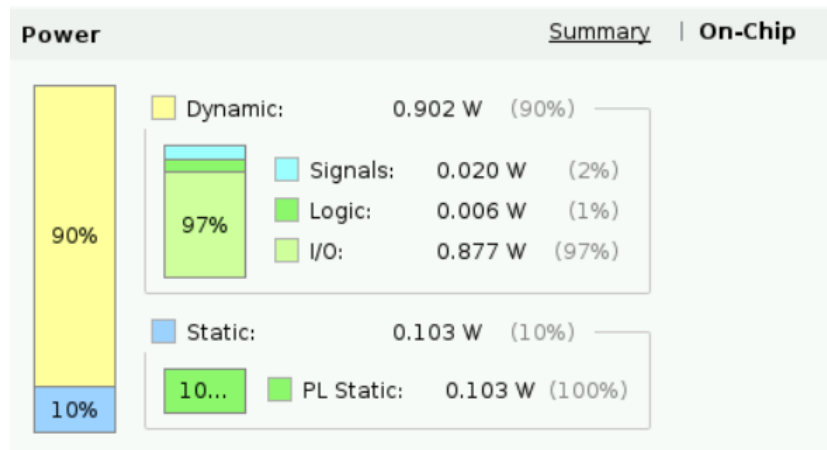

## Post Synthesis Utilization

Utilization


Post-Synthesis | Post-Implementation

Graph | Table


| Resource | Estimation | Available | Utilization % |
|----------|------------|-----------|---------------|
| LUT      | 1          | 17600     | 0.01          |
| IO       | 5          | 100       | 5.00          |

# Ripple Adder

## Ripple Adder RTL

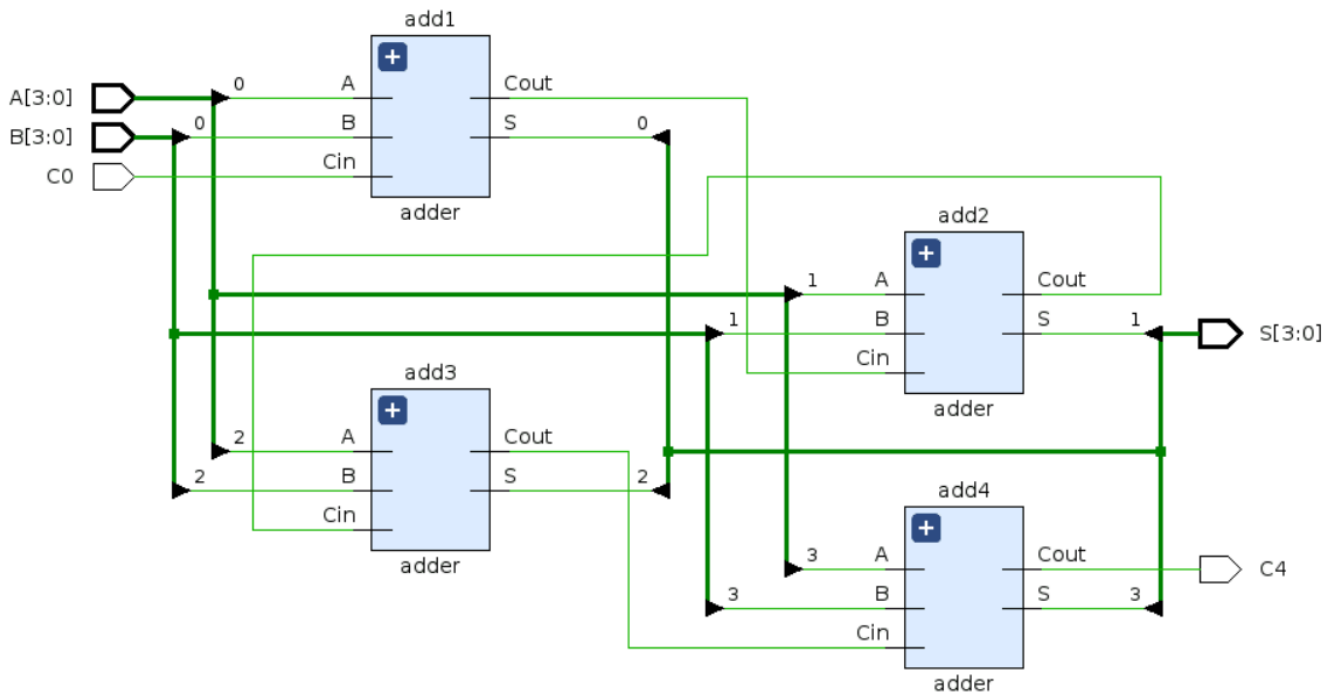

## Ripple Adder Synthesis Schematic

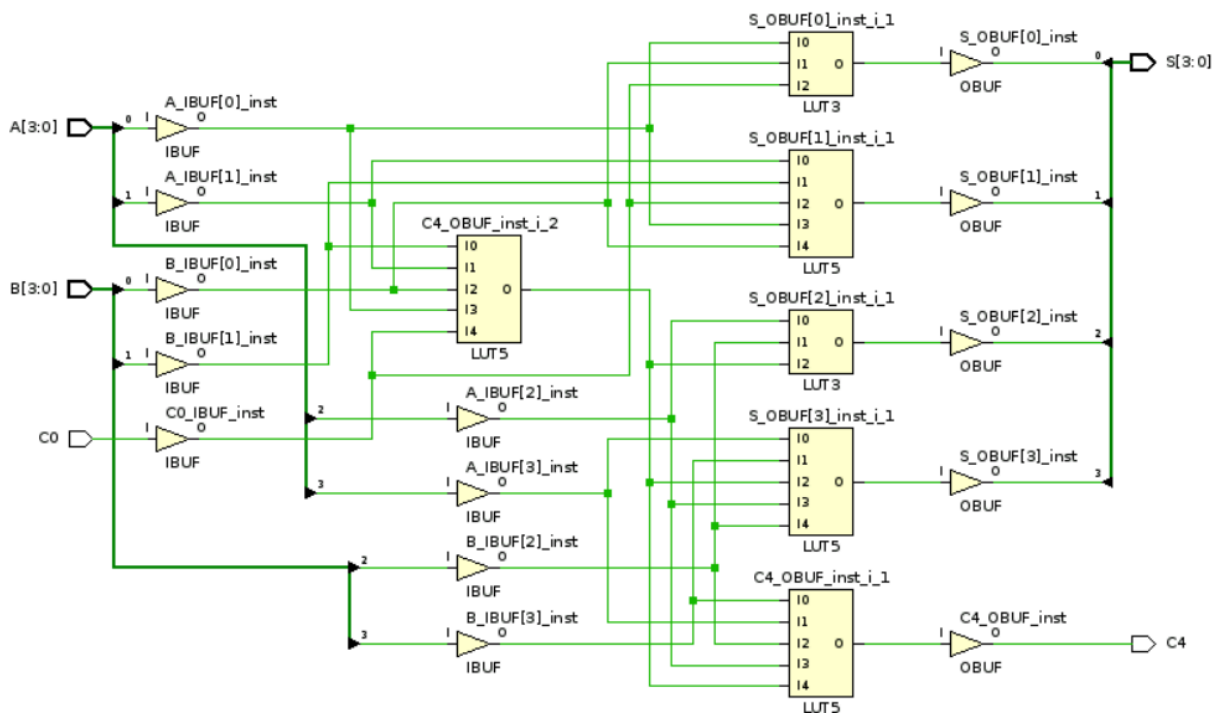

Ripple Adder Utilization Table


| Utilization |            | Post-Synthesis   Post-Implementation |               |
|-------------|------------|--------------------------------------|---------------|
|             |            | Graph   <b>Table</b>                 |               |
| Resource    | Estimation | Available                            | Utilization % |
| LUT         | 4          | 17600                                | 0.02          |
| I/O         | 14         | 100                                  | 14.00         |

Ripple Adder Power Graph




ALU

ALU RTL Schematic

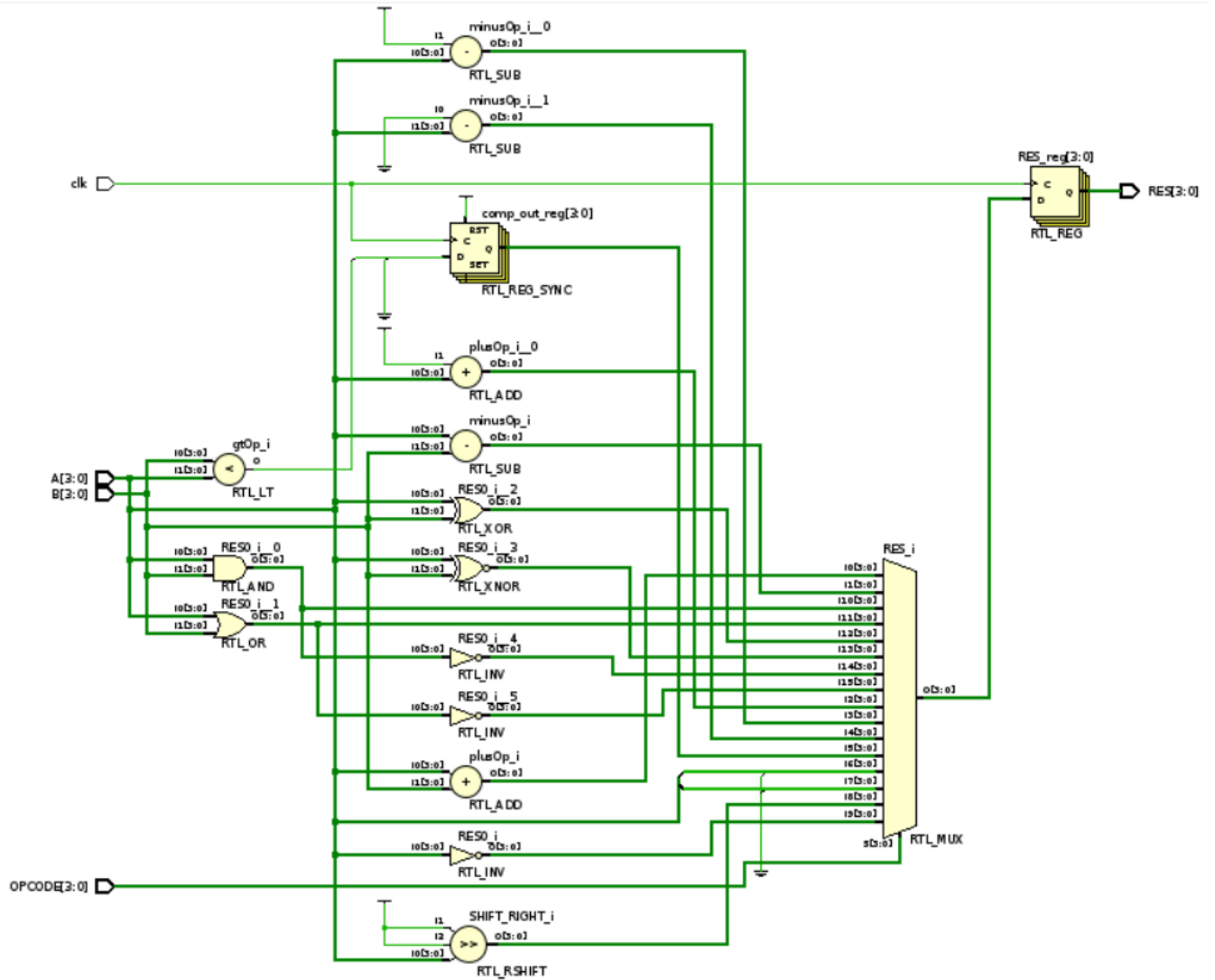

ALU Synthesis Graph

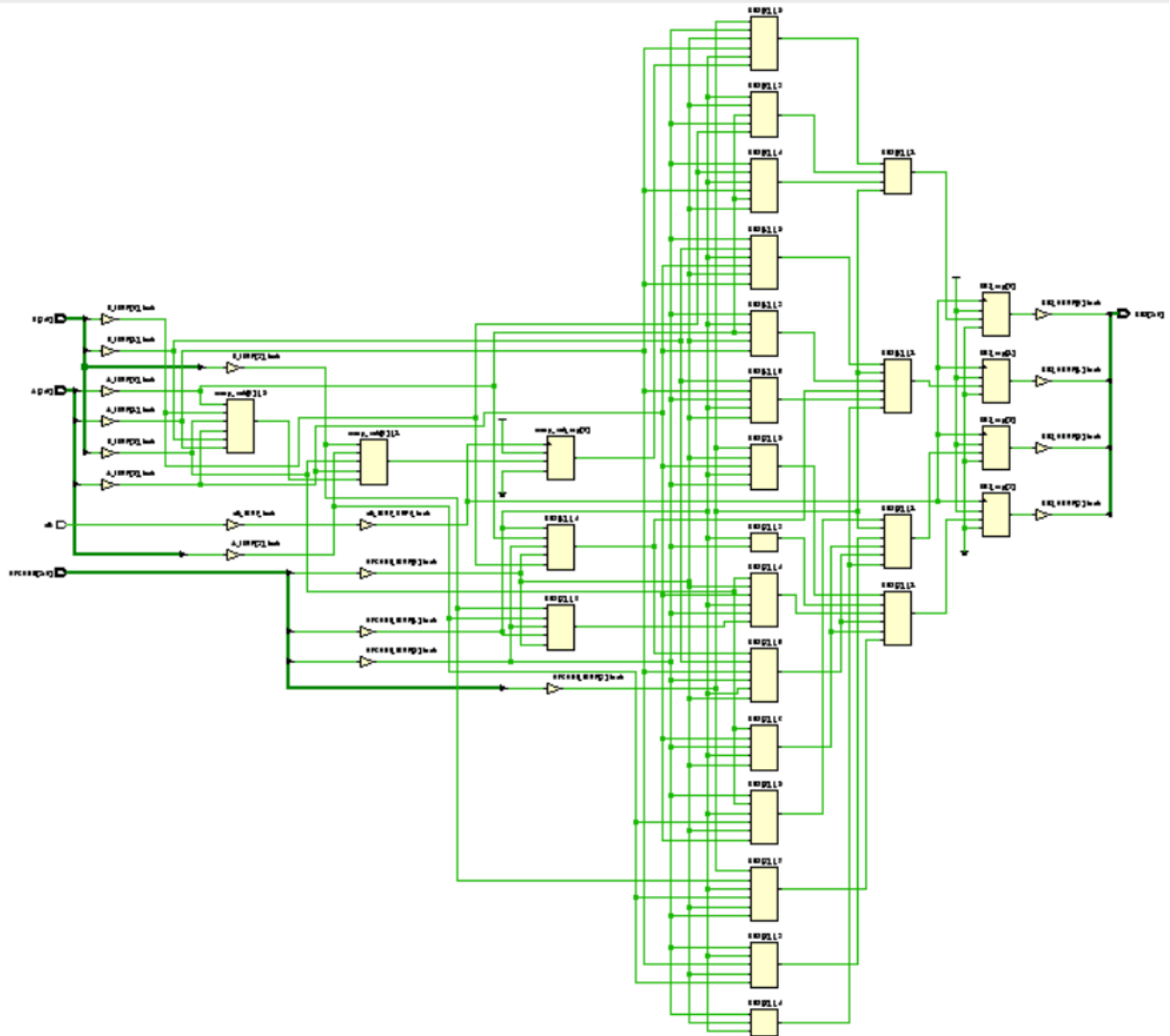

ALU Synthesis Table

## Utilization

Post-Synthesis | Post-Implementation


Graph | **Table**

| Resource | Estimation | Available | Utilization % |
|----------|------------|-----------|---------------|
| LUT      | 59         | 17600     | 0.34          |
| FF       | 109        | 35200     | 0.31          |
| IO       | 13         | 100       | 13.00         |
| BUFG     | 1          | 32        | 3.13          |

## ALU Power Graph

### Power


Summary | **On-Chip**

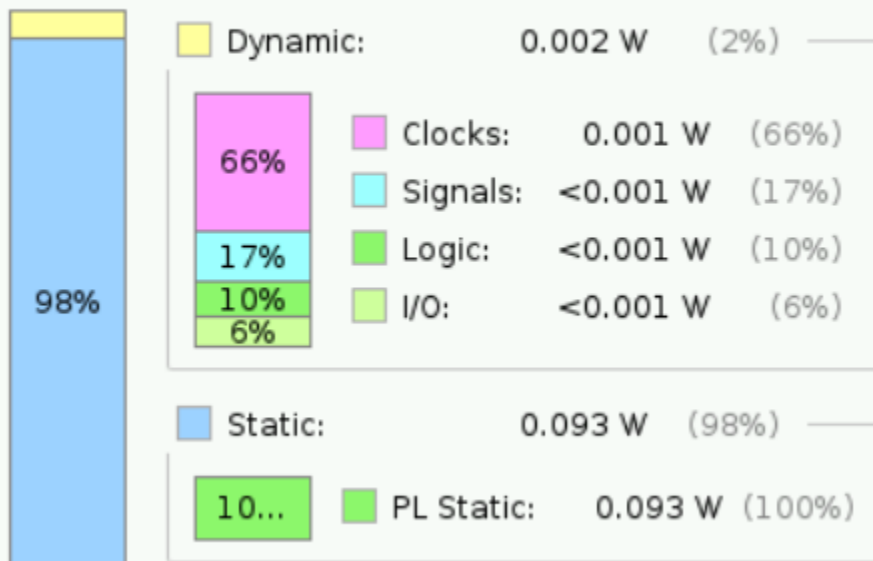




## ALU\_Tester

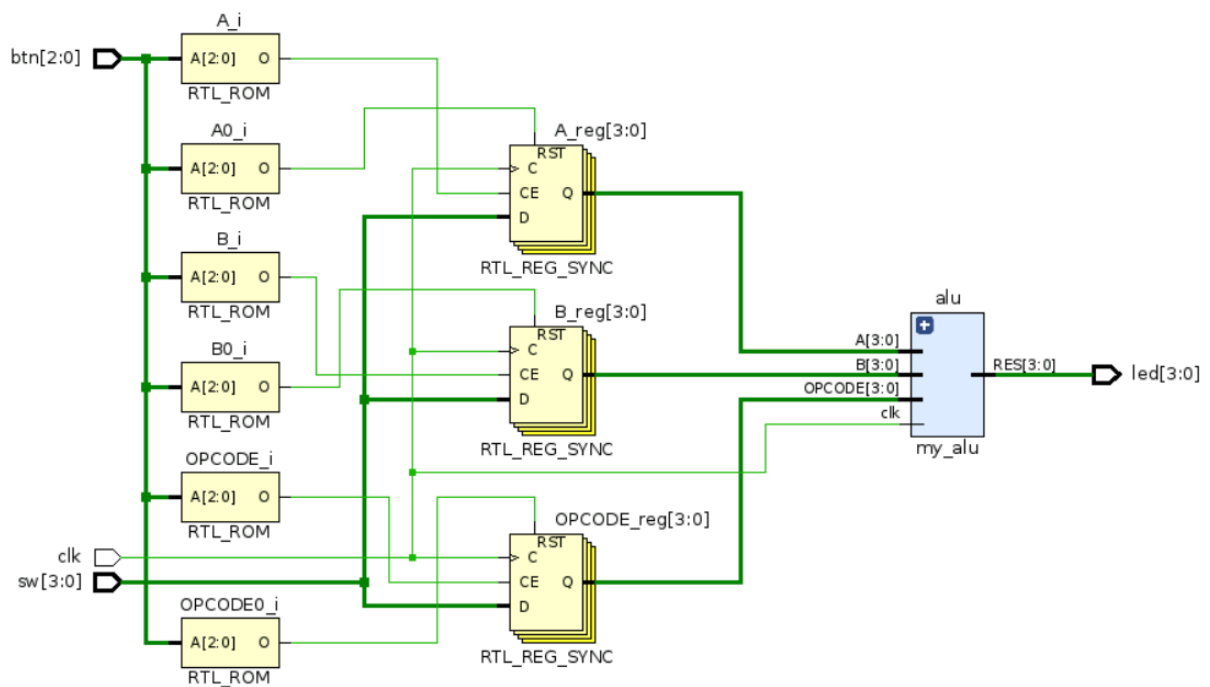
### ALU\_Tester RTL Used for Simulation, without debouncers



### ALU\_Tester with Debouncers:

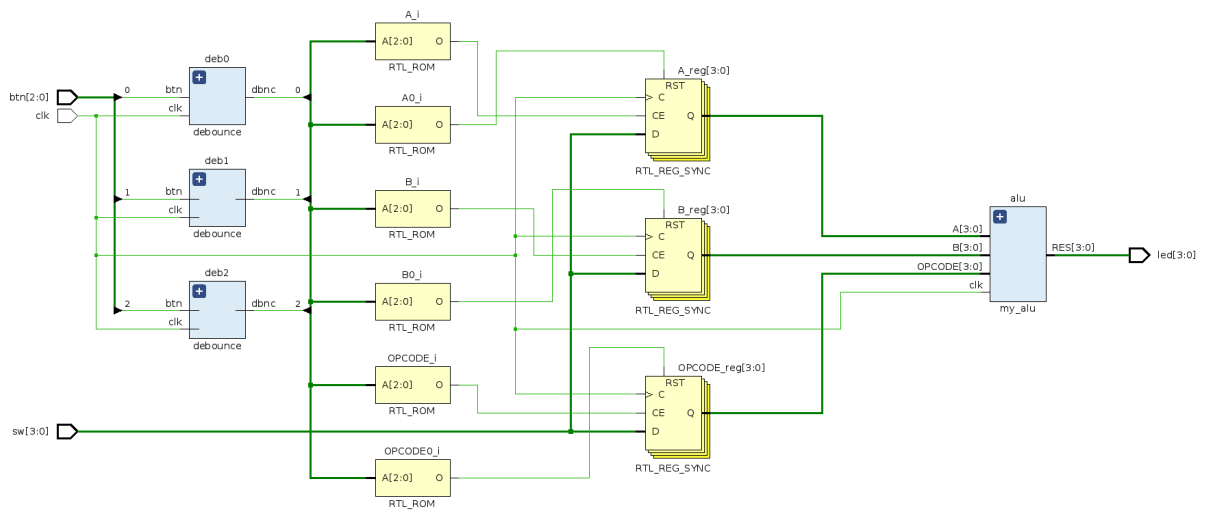


**ALU\_Tester Synthesis Schematic**

 

Post Synthesis Utilization Table

| Utilization | Post-Synthesis   Post-Implementation |           |               |  |
|-------------|--------------------------------------|-----------|---------------|--|
|             | Graph   Table                        |           |               |  |
| Resource    | Estimation                           | Available | Utilization % |  |
| LUT         | 59                                   | 17600     | 0.34          |  |
| FF          | 109                                  | 35200     | 0.31          |  |
| IO          | 13                                   | 100       | 13.00         |  |
| BUFG        | 1                                    | 32        | 3.13          |  |

## Post Implementation On Chip Graph

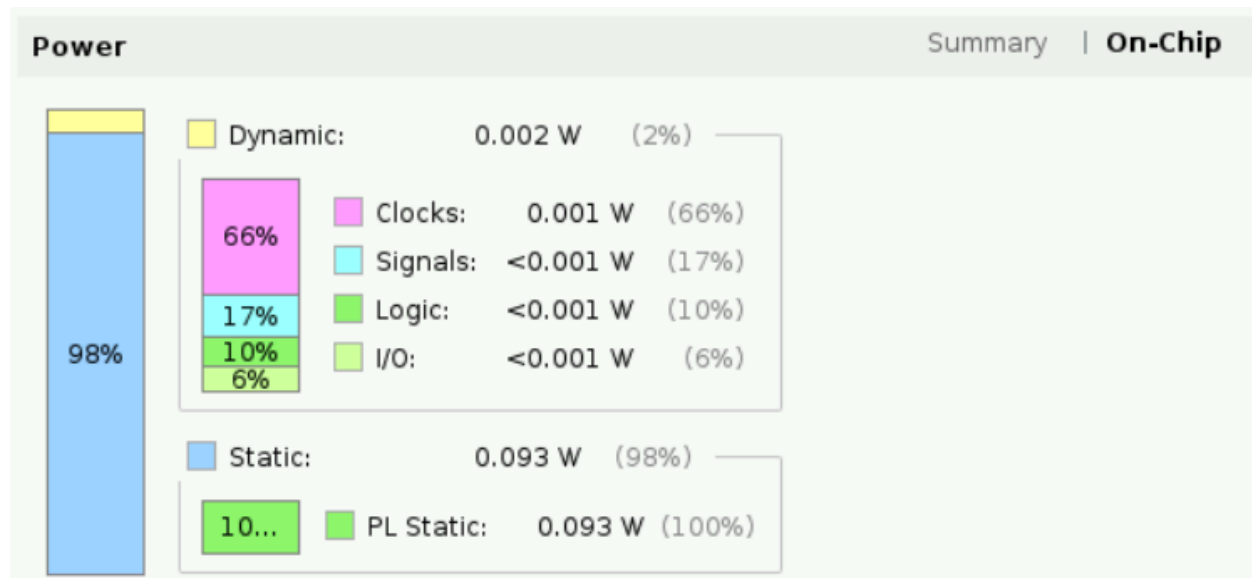

*For the XDC file, it was required to uncomment the buttons and switches and clock as inputs, and the LEDs as outputs.*

## Answers to Additional Questions and Extra Credit:

### Pre Lab - Operators and Conversions Review


- Write the logic equations for a single bit full adder with inputs A, B, Cin, and outputs Y, Cout.

$\text{xorAB} \leq A \text{ xor } B;$


$Y \leq \text{Cin xor xorAB} ;$

$\text{Cout} \leq (A \text{ and } B) \text{ or } (\text{Cin and xorAB});$

 - Draw a black box diagram for the single bit full adder described above.



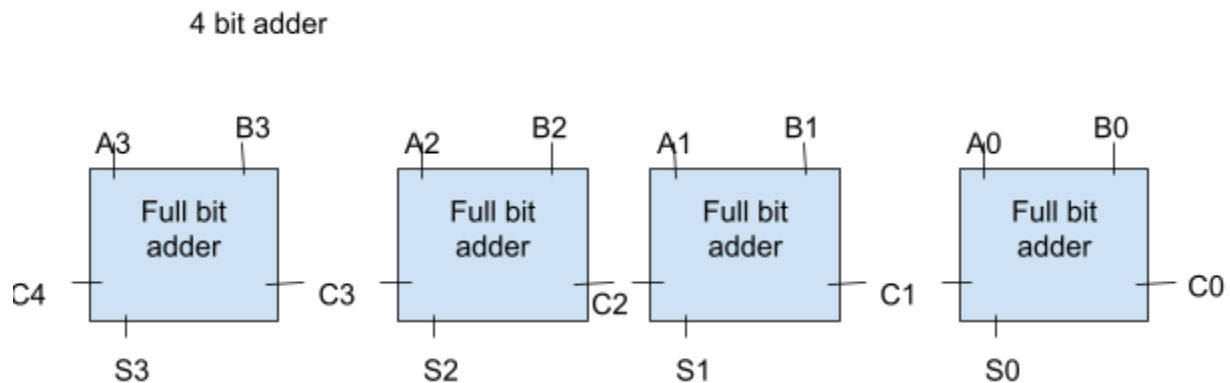- Draw a block diagram of a 4-bit ripple-carry adder showing the inner connectivity among the single bit full adders, with 4 bit bus inputs A and B, a single bit input Cin, a 4-bit bus output S, and a single bit output Cout. The ports of the top level diagram are: A, B, S, Cin, Cout.



**Conclusion:** I learned in this lab that how you code a program influences how state impacts calculations at the level of single clock ticks. In my simulation waveforms, state is only considered from times before the clock tick, not at the time of the clock tick(when state might be updated).

**Follow Up:** I feel like I understand test benching, but can do better in working with unsigned and signed calculation.